

Automotive Bridge Sensor Conditioner Based on NSC9260X

AN-12-0022

Author: Feifei Sun



Automotive Bridge Sensor Conditioner Based on NSC9260X

ABSTRACT

The NSC9260X is a highly integrated and AEC-Q100 qualified IC for capacitive sensor conditioning. The NSC9260X integrates a C/V converter, a 24-bit ADC for primary signal measurement channel, a 24-bit ADC for temperature measurement channel and sensor calibration logic. With the calibration algorithm built in the internal MCU, the NSC9260X supports to compensate sensor offset, sensitivity, temperature drift up to 2nd order, and non-linearity up to the 3rd order. The calibration coefficients are stored in a 64-Byte EEPROM that can be programmed multiple times. The NSC9260X also supports Over-voltage and Reverse-voltage protection. It can provide analog output and PWM output. It can also support sensor diagnosis.

INDEX

1. PIN CONFIGURATION AND FUNCTIONS	2
2. FUNCTION	3
2.1. SENSOR EXCITATION MODULE	3
2.2. TEMPERATURE SENSOR MODULE	4
2.3. ANALOG OUTPUT MODE	4
3. APPLICATION	4
3.1. ANALOG VOLTAGE OUTPUT	4
3.2. ANALOG VOLTAGE OUTPUT WITH HIGH VOLTAGE INPUT	6
3.3. ANALOG VOLTAGE OUTPUT WITH HIGH VOLTAGE INPUT (BJT)	7
4. REVISION HISTORY	9

Automotive Bridge Sensor Conditioner Based on NSC9260X

1.Pin Configuration and Functions

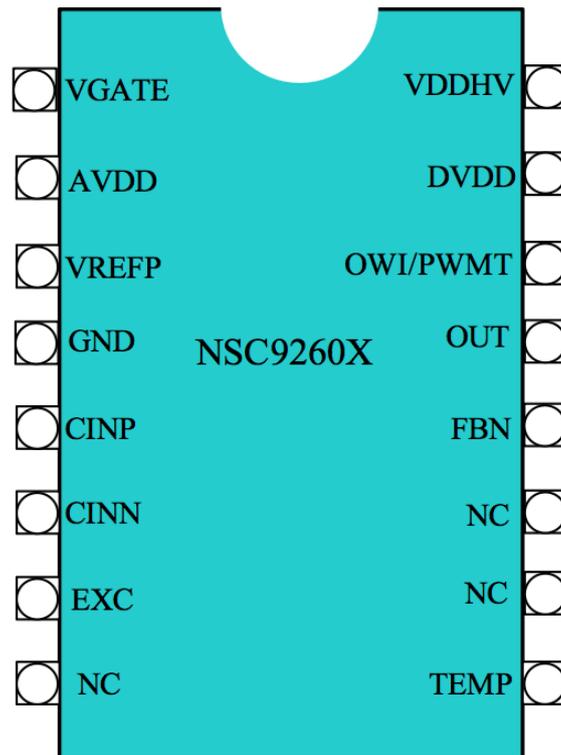


Figure 1.1 NSC9260X Pin

Table 1.1 NSC9260X Pin Configuration and Description

PIN NO.	SYMBOL	FUNCTION
1	VGATE	JFET controller output
2	AVDD	Internal analog power supply
3	VREFP	Internal Reference voltage VREF output/External Reference voltage input(set by register 0xA2)
4	GND	Ground
5	CINP	Capacitance measurement channel input positive
6	CINN	Capacitance measurement channel input negative

Automotive Bridge Sensor Conditioner Based on NSC9260X

PIN NO.	SYMBOL	FUNCTION
7	EXC	Output excitation source
8	NC	Floating
9	TEMP	External temperature sensor input
10	NC	Floating
11	NC	Floating
12	FBN	Output driver feedback
13	OUT/PWMDAC	Driver output or DAC PWM output
14	OWI/PWMT	One-wire interface or Temperature channel PWM output
15	DVDD	1.8V digital supply from internal LDO
16	VDDHV	Power supply with OVP/RVP

2.Function

2.1.Sensor Excitation Module

The NSC9260X uses a square wave signal as the excitation source for measuring capacitance. The capacitor input pins can be used as differential connection or single end connection. The differential input capacitors' common pin is driven by the EXC pin. CINP and CINN connect to the other side of those two capacitors of the capacitive sensor. If single end connection is used, connect the capacitor to CINP pin.

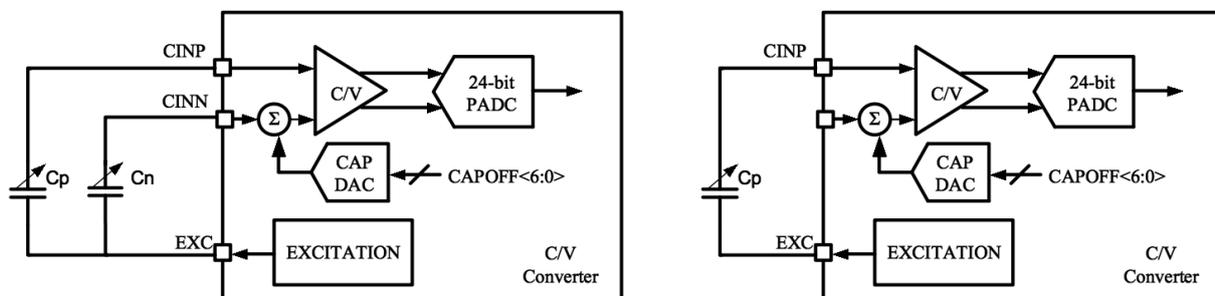


Figure 2.1 Capacitive Sensor Connection Diagram

Automotive Bridge Sensor Conditioner Based on NSC9260X

The chip is powered by VDDHV and supports -24~28V(1Hour, 70 °C) over voltage and reverse voltage protection.

The bi-directional transient voltage suppression diode D1 (SD15C) protects against ESD and other high voltage transients. SD15C can withstand 15V continuous over voltage and clamp the voltage at 24V at IPP=1A, tp=8/20μs to protect the chip from high voltage damage. If the EMC environment of the application is more severe, this TVS can be replaced with a higher power TVS at the cost of a larger package size.

The TVS diode D2 (SD05C) on VOUT port protects the OWI, OUT and FBN pins from damage by transient high voltage pulses. These TVS diodes should be placed as close to the connector as possible. It is better to place TVS diode through the trace between connector and chip pin. This will make signal to pass through TVS diode before reaching pin of the chip and provide better protection.

C1, C2 capacitors connected between the system power and ground and the chassis ground make the shell and the system power and ground has an AC low impedance, can play the role of anti-interference of high frequency. These 2 capacitors should be close to the PCB board and the shell connection. In some cases, the housing is required to have some high voltage isolation of the connector pins, In that case, these 2 capacitors need to be selected with the right voltage withstand capability.

FB1, FB2 are very effective for protection against high frequency interference. Place these 2 beads close to the connector too.

C3 capacitors filter out power supply noise and keep the power input stable. This capacitor is placed as close to the chip pins as possible, so that the power line passes through the capacitor before reaching the chip pins. The capacitance value may be increased or capacitor with different values may be added depending on the test level in the EMC real test.

C6, C7 improve the noise immunity of the system and make the output more stable. R1, R2 in the output stage can help to protect high voltage and limit the current forced into chip pins.

Table 3.1 BOM of Analog Voltage Output Schematic

Comment	Designator	Footprint	Value
Cap	C1	0603 (or larger)	100nF(100V or larger)
Cap	C2	0603 (or larger)	100nF(100V or larger)
Cap	C3	0603	100nF
Cap	C6	0603	47nF
Cap	C7	0603	47nF
Bead	FB1	0603	BLM18AG102SH1D
Bead	FB2	0603	BLM18AG102SH1D
Res	R1	0603	100
Res	R2	0603	1K
TVS	D1	SOD323	SD15C-01FTG
TVS	D2	SOD323	SD05C-01FTG
IC	U1	SSOP16	NSC9260X

Automotive Bridge Sensor Conditioner Based on NSC9260X

Similar to the application in Figure 3.2, a NPN BJT with a 51 kohm resistor can also be used for the high voltage regulation. An extra zener diode is recommended to be mounted on VGATE pin to protect against high voltage.

Table 3.3 BOM of Analog Voltage Output with High Voltage Input (BJT) Schematic

Comment	Designator	Footprint	Value
Cap	C1	0603 (or larger)	100nF(100V or larger)
Cap	C2	0603 (or larger)	100nF(100V or larger)
Cap	C3	0603	1uF
Cap	C6	0603	100nF
Cap	C7	0603	47nF
Bead	FB1	0603	BLM18AG102SH1D
Bead	FB2	0603	BLM18AG102SH1D
Res	R1	0603	100
Res	R2	0603	1K
Res	R5	0603	51K
TVS	D1	SOD323	SD36C-01FTG
TVS	D2	SOD323	SD05C-01FTG
Diode	D3	SOD323	BAT46WJ
Diode	D4	SOD323	SZMM3Z6V2ST1G
Transistor	Q1	SOT23 (or SOT223)	BC846 (or BCP56)
IC	U1	SSOP16	NSC9260X

Automotive Bridge Sensor Conditioner Based on NSC9260X

4.Revision History

Revision	Description	Author	Date
1.0	Initial version	Feifei Sun	16/6/2023

Sales Contact: sales@novosns.com; Further Information: www.novosns.com

IMPORTANT NOTICE

The information given in this document (the “Document”) shall in no event be regarded as any warranty or authorization of, express or implied, including but not limited to accuracy, completeness, merchantability, fitness for a particular purpose or infringement of any third party’s intellectual property rights.

Users of this Document shall be solely responsible for the use of NOVOSENSE’s products and applications, and for the safety thereof. Users shall comply with all laws, regulations and requirements related to NOVOSENSE’s products and applications, although information or support related to any application may still be provided by NOVOSENSE.

This Document is provided on an “AS IS” basis, and is intended only for skilled developers designing with NOVOSENSE’ products. NOVOSENSE reserves the rights to make corrections, modifications, enhancements, improvements or other changes to the products and services provided without notice. NOVOSENSE authorizes users to use this Document exclusively for the development of relevant applications or systems designed to integrate NOVOSENSE’s products. No license to any intellectual property rights of NOVOSENSE is granted by implication or otherwise. Using this Document for any other purpose, or any unauthorized reproduction or display of this Document is strictly prohibited. In no event shall NOVOSENSE be liable for any claims, damages, costs, losses or liabilities arising out of or in connection with this Document or the use of this Document.

For further information on applications, products and technologies, please contact NOVOSENSE (www.novosns.com).

Suzhou NOVOSENSE Microelectronics Co., Ltd